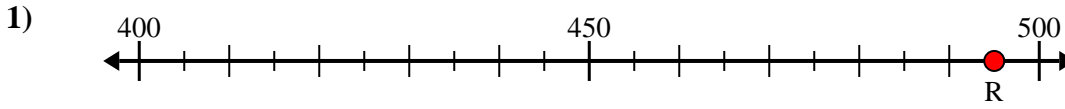




Find the value of R.


Answers




1. \_\_\_\_\_




2. \_\_\_\_\_

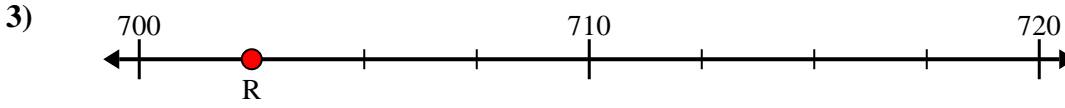


3. \_\_\_\_\_

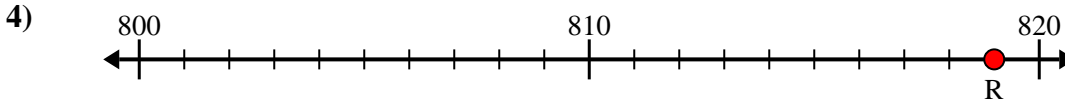

4. \_\_\_\_\_

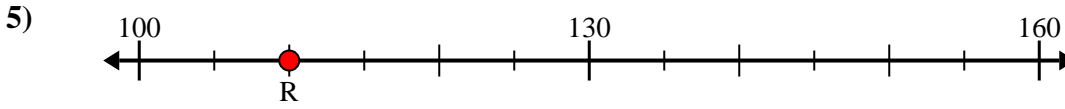


5. \_\_\_\_\_

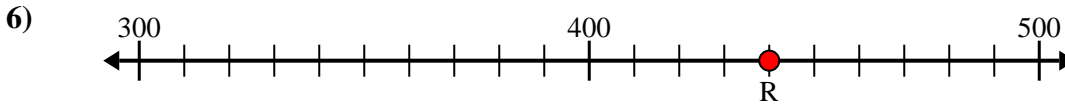


6. \_\_\_\_\_




7. \_\_\_\_\_

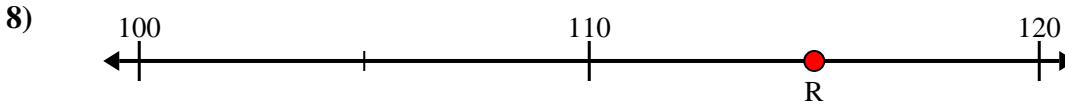

8. \_\_\_\_\_

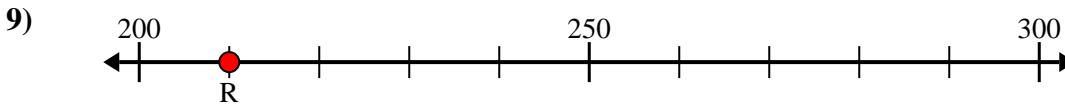











9. \_\_\_\_\_

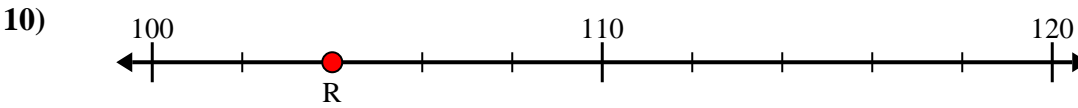

10. \_\_\_\_\_



Find the value of R.

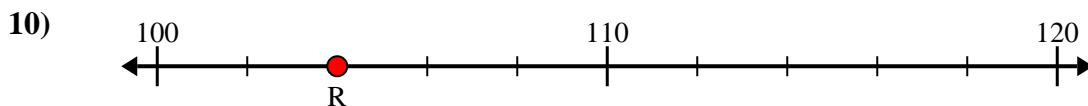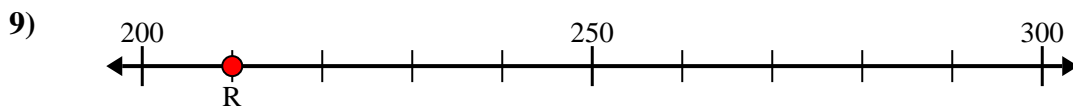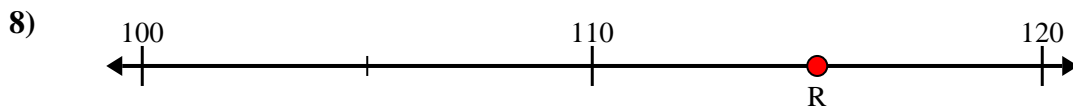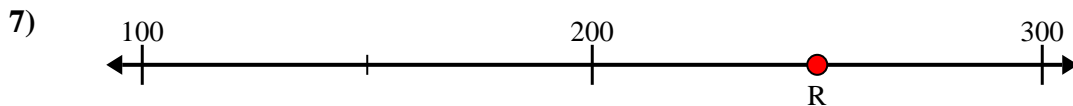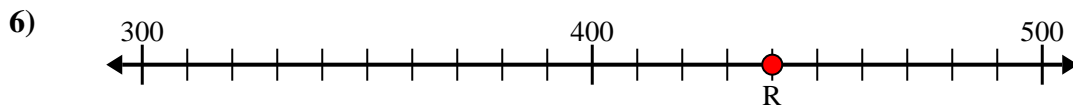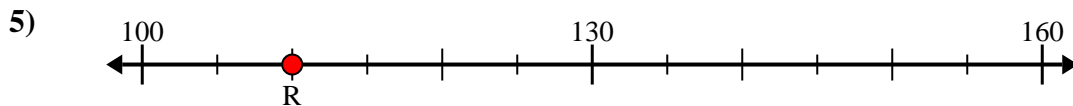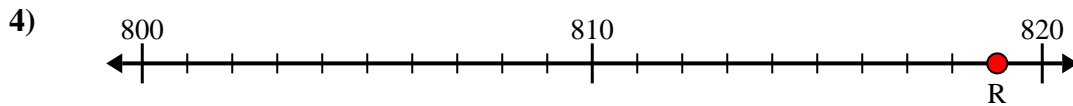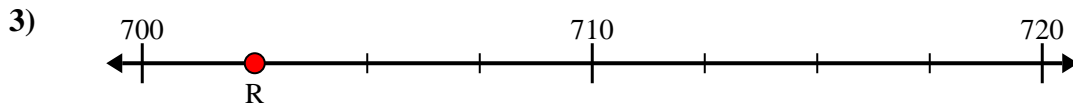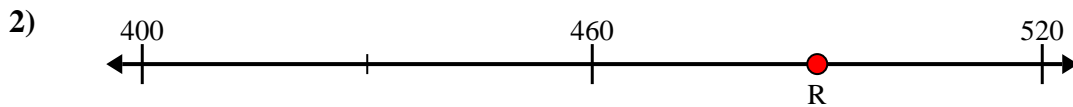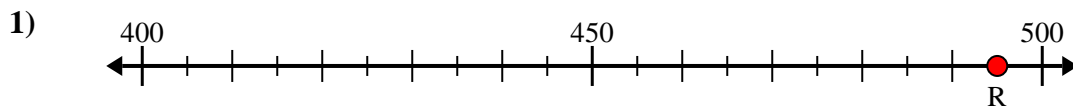

Answers

1. 495

2. 490

3. 702.5

4. 819

5. 110

6. 440

7. 250

8. 115

9. 210

10. 104