
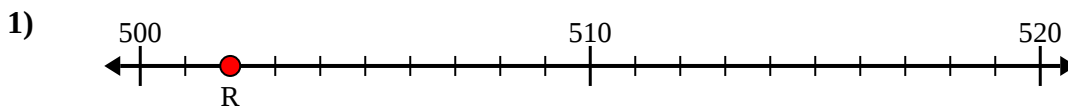


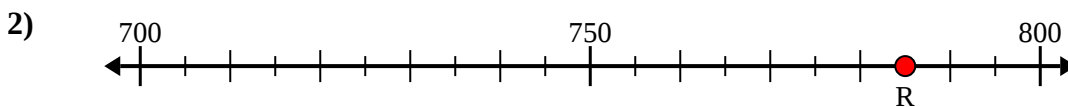


Find the value of R.

Answers


1. \_\_\_\_\_




2. \_\_\_\_\_

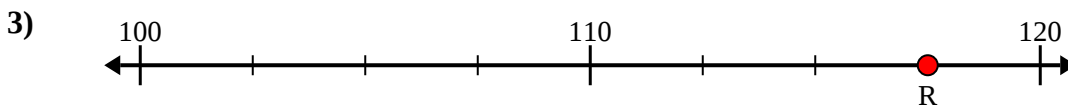


3. \_\_\_\_\_

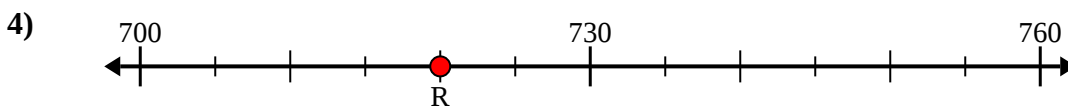


4. \_\_\_\_\_

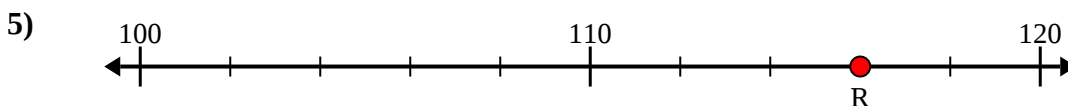


5. \_\_\_\_\_

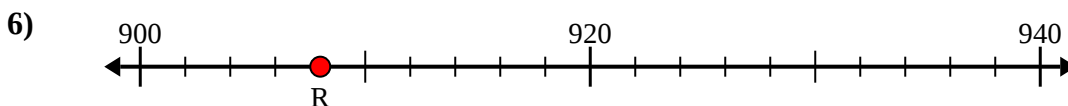


6. \_\_\_\_\_

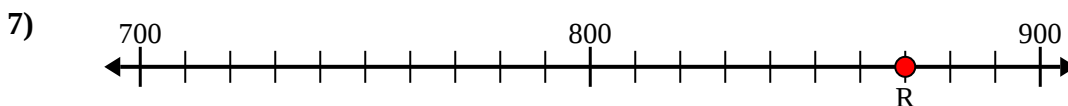


7. \_\_\_\_\_

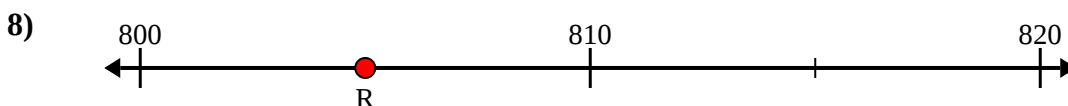

8. \_\_\_\_\_

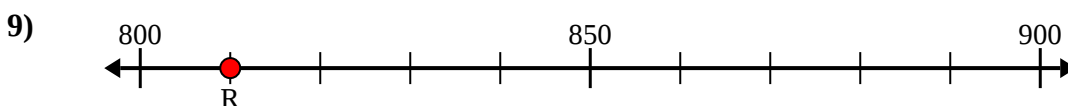











9. \_\_\_\_\_

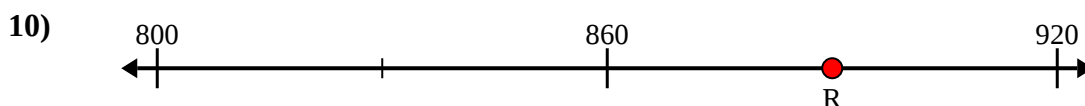

10. \_\_\_\_\_



Find the value of R.

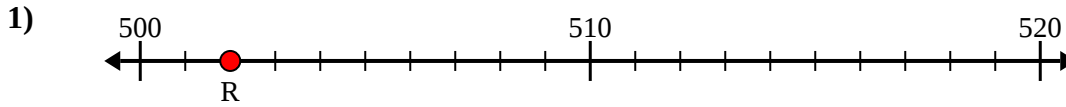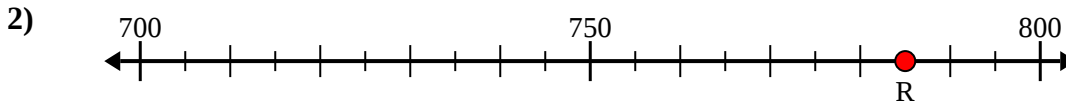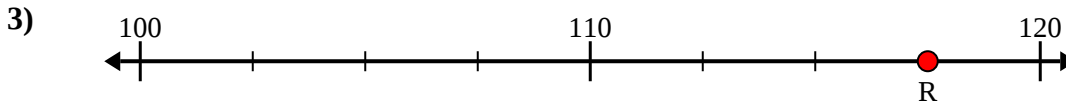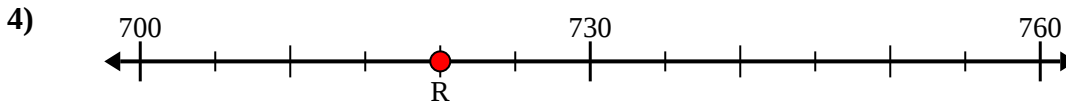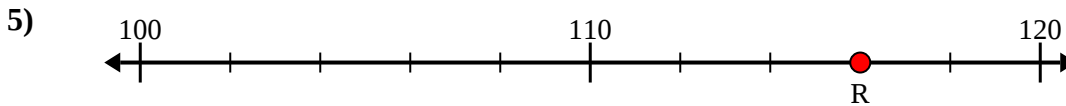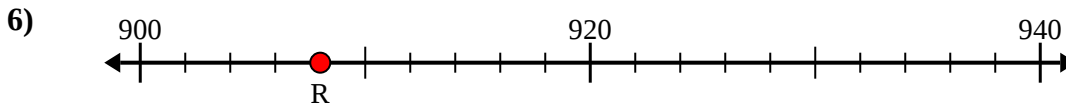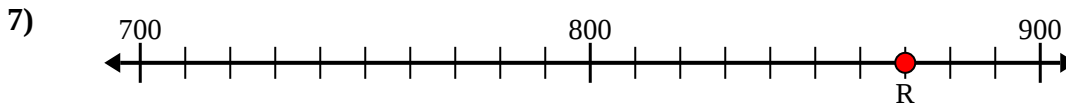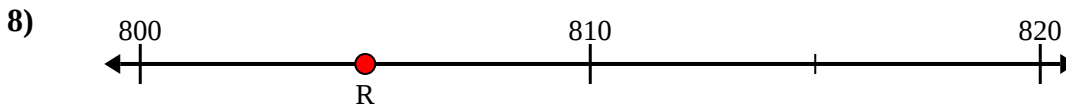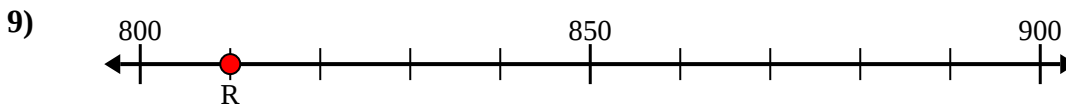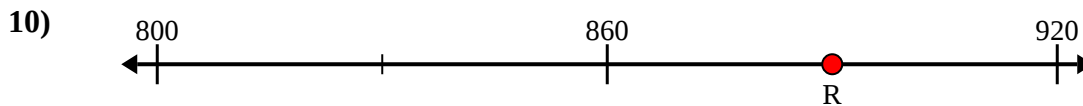Answers1. 5022. 7853. 117.54. 7205. 1166. 9087. 8708. 8059. 81010. 890