
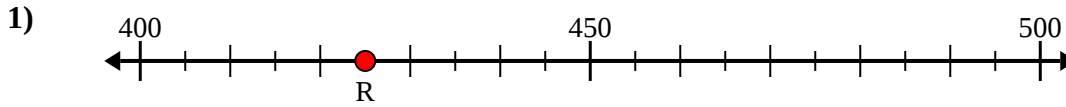


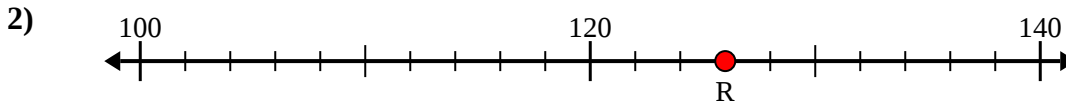


Find the value of R.

Answers


1. _____




2. _____

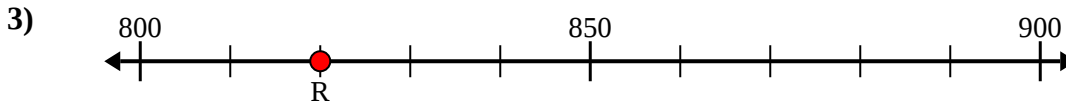


3. _____

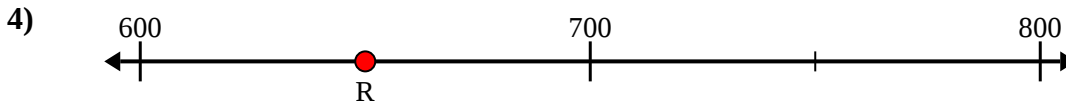


4. _____

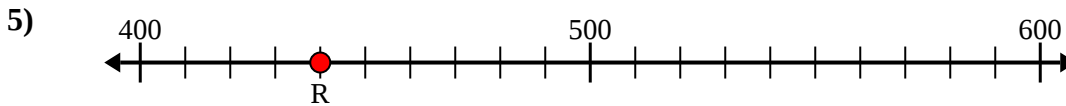


5. _____

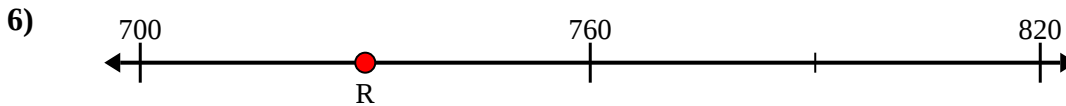


6. _____

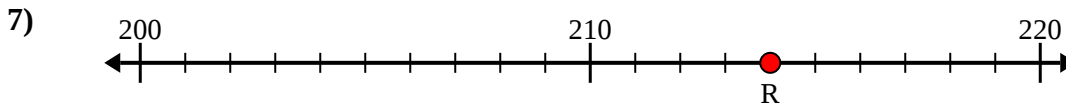


7. _____

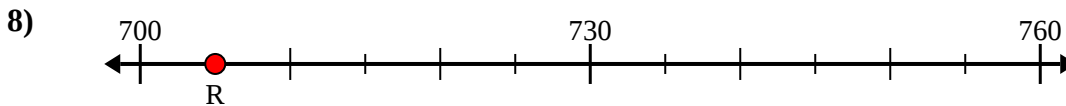

8. _____

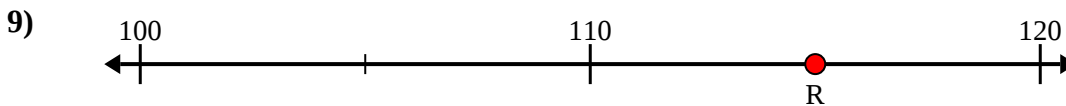











9. _____

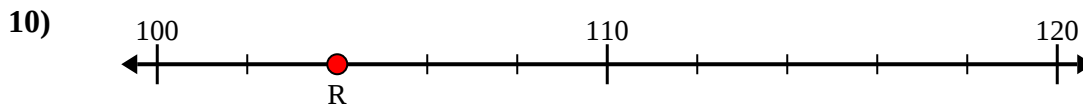

10. _____



Find the value of R.

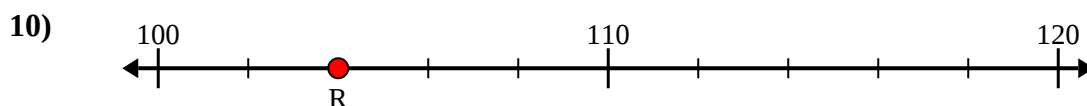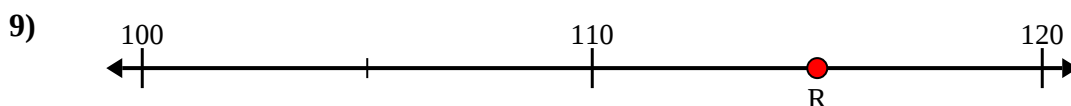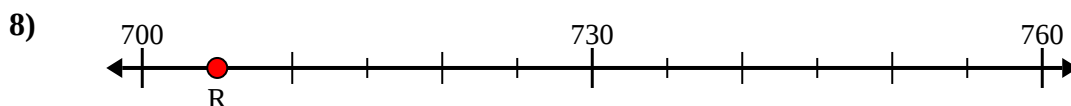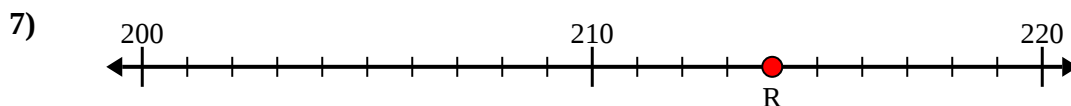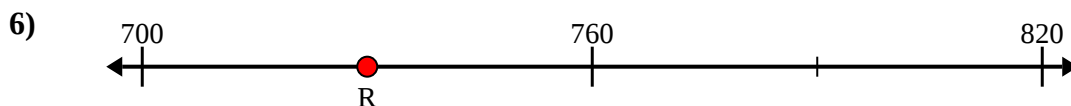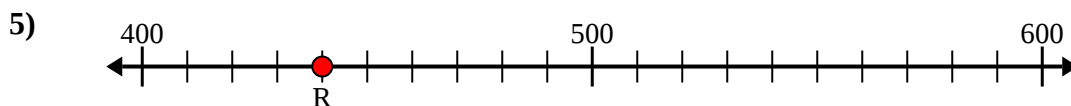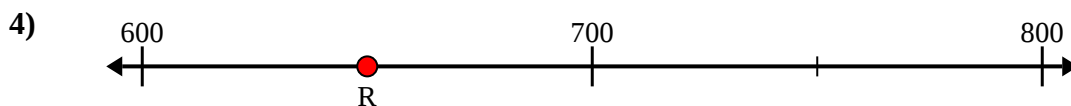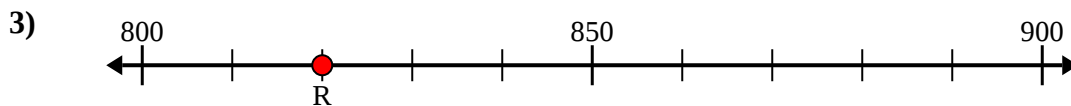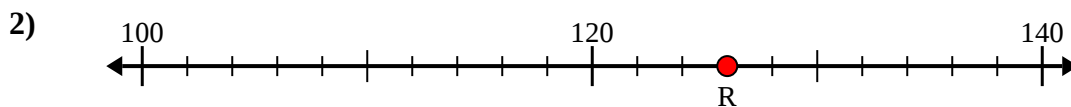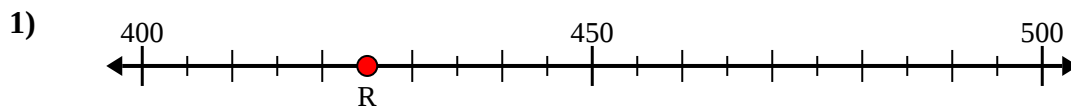**Answers**1. **425**2. **126**3. **820**4. **650**5. **440**6. **730**7. **214**8. **705**9. **115**10. **104**